

COMMON EQNS:

$$I = \frac{V}{R} = \frac{P}{V} \quad I = \frac{P}{V} = \frac{P}{V}$$

$$V_o = V_i \left( \frac{R_2}{R_1 + R_2} \right)$$

$$V_{rms} = \frac{1}{\sqrt{2}} V$$


NASH

ECE 3813




TEST 1 NOTE SHEET

# OPERATIONAL AMPLIFIERS


INVERTING

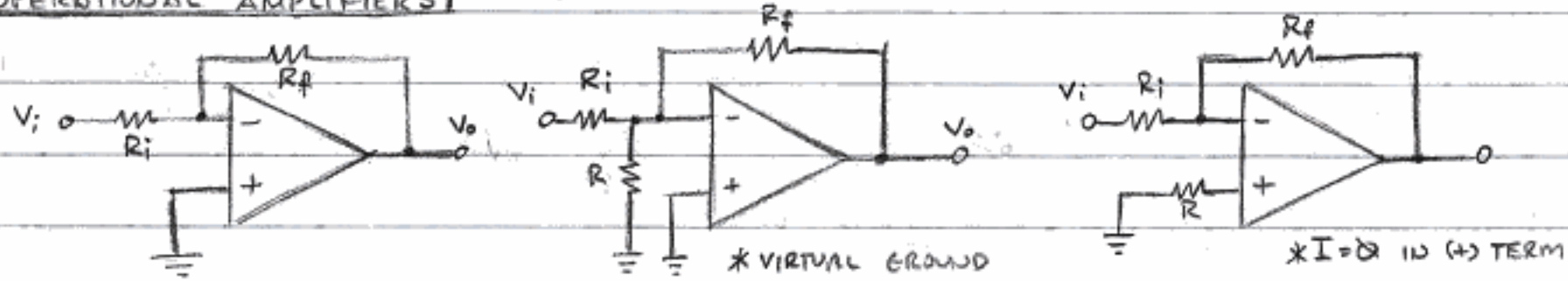


NON-INVERTING

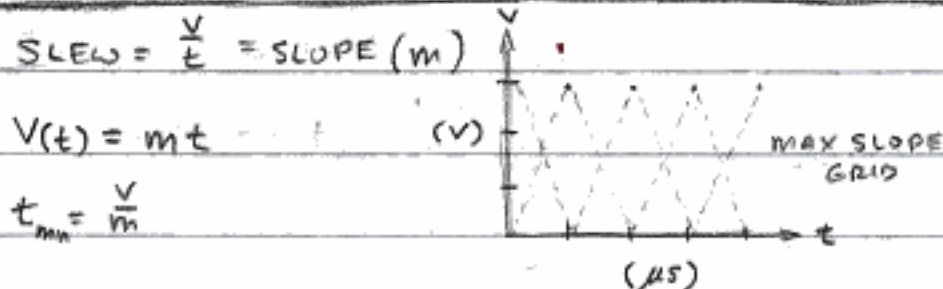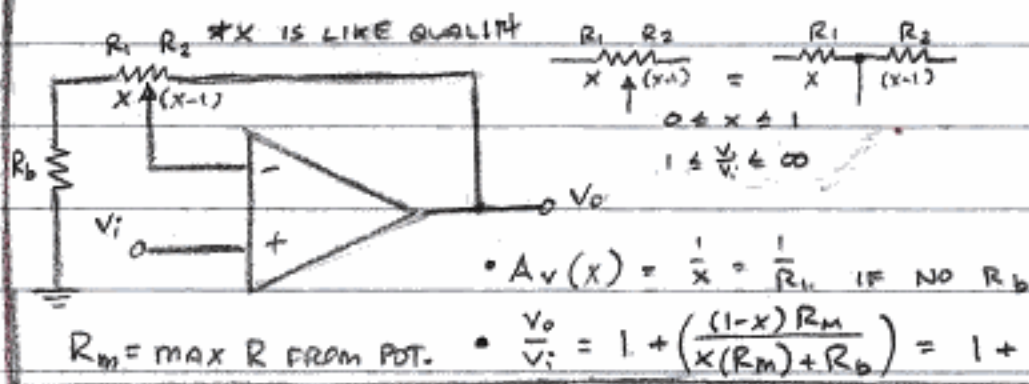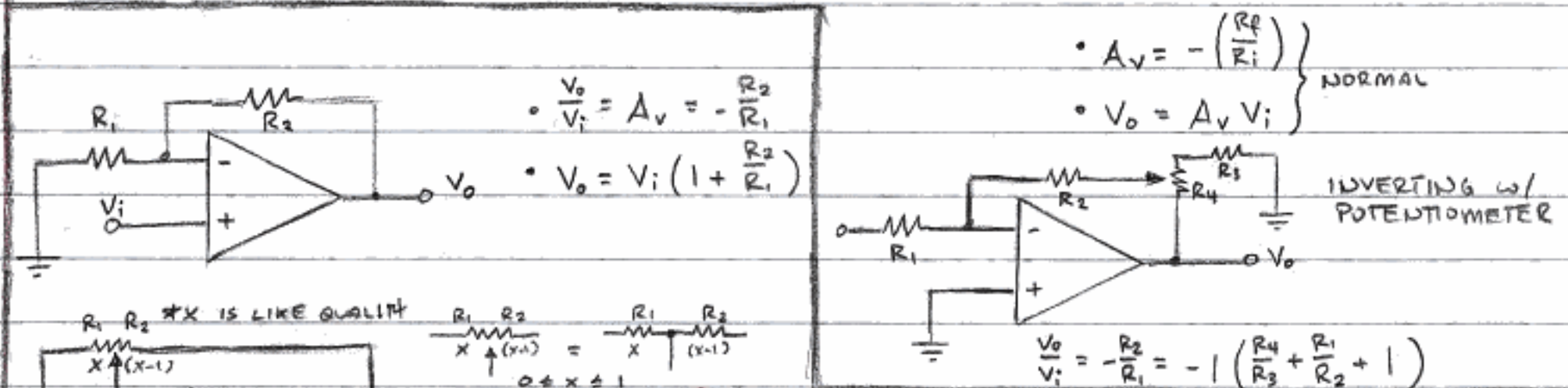

NOTABLE CONFIGURATIONS

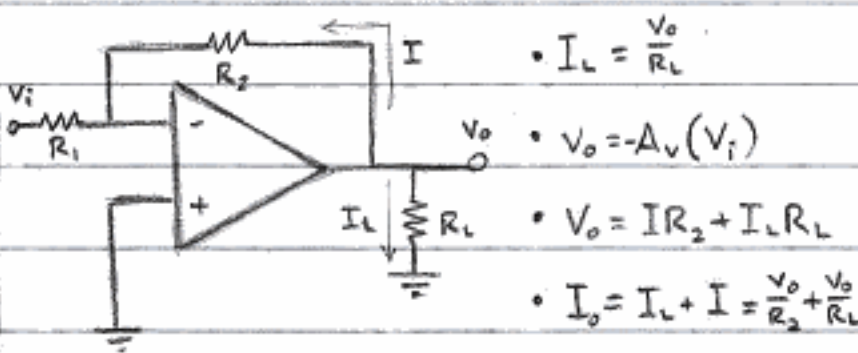


SUMMING AMPS

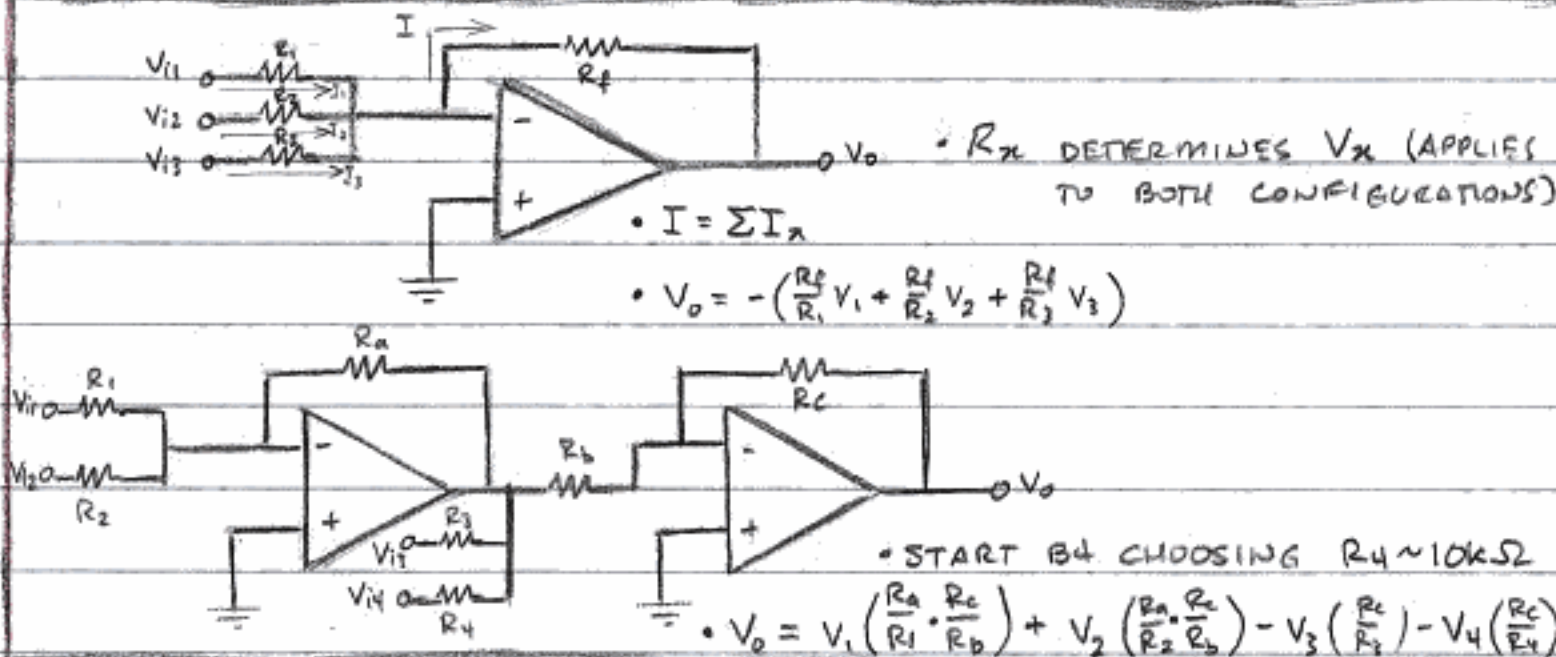

IDEAL AMPS HAVE HIGH  $R_i$ /LOW  $R_o$   
CLOSED-LOOP AMPS:  $A_v \sim 1$   
DIFF. AMP IDEAL TO ELIM. "HUM"  
RMS ONLY FOR POWER CALCULATION

DIFFERENCE AMP

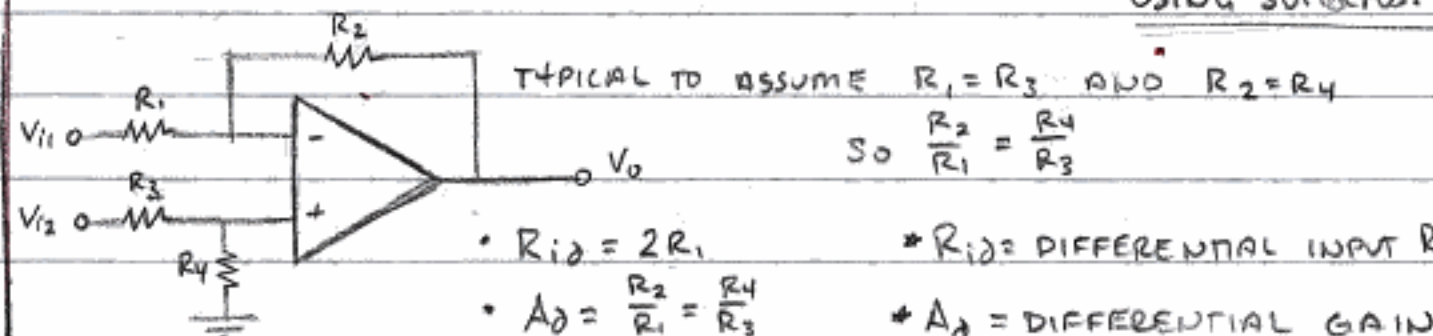


USING SUPERPOS: 1. SET  $V_{i1}$  TO G, CALC  $V_{i2} \rightarrow V_{o1} = \left( \frac{R_2}{R_1} \right) V_{i1}$   
2. SET  $V_{i2}$  TO G, CALC  $V_{i1} \rightarrow V_{o2} = V_{i2} \left( \frac{R_2}{R_1} \right)$   
3. CALC.  $V_{id} \rightarrow V_o = \frac{R_2}{R_1} (V_{i2} - V_{i1}) = \frac{R_2}{R_1} V_{id}$   
4. CALC DIFF. GAIN  $\rightarrow A_d = \frac{2R_2}{R_1} = \frac{2R_4}{R_3}$

CMRR =  $\frac{A_d}{A_{cm}}$   
CMRR =  $20 \log \left( \frac{A_d}{A_{cm}} \right)$   
CMRR = COMMON MODE REJECTION RATIO; MEASURES ABILITY OF AMP TO ACCURATELY CANCEL VOLTAGES
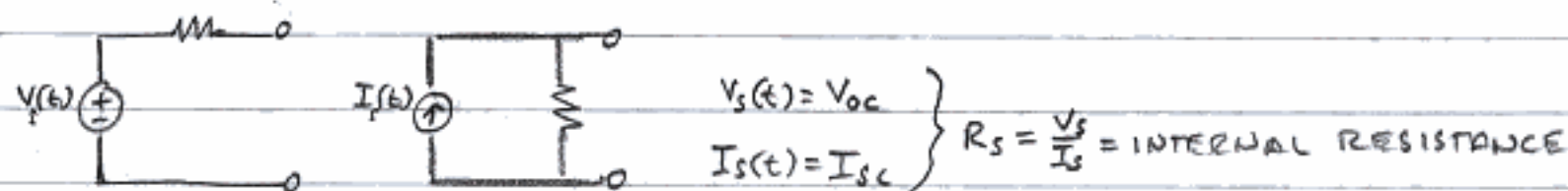
## SIGNALS


THEVENIN EQUIVALENT: OPEN CIRCUIT VOLTAGE FROM A VOLTAGE SOURCE

NORTON EQUIVALENT: SHORT CIRCUIT CURRENT FROM A CURRENT SOURCE


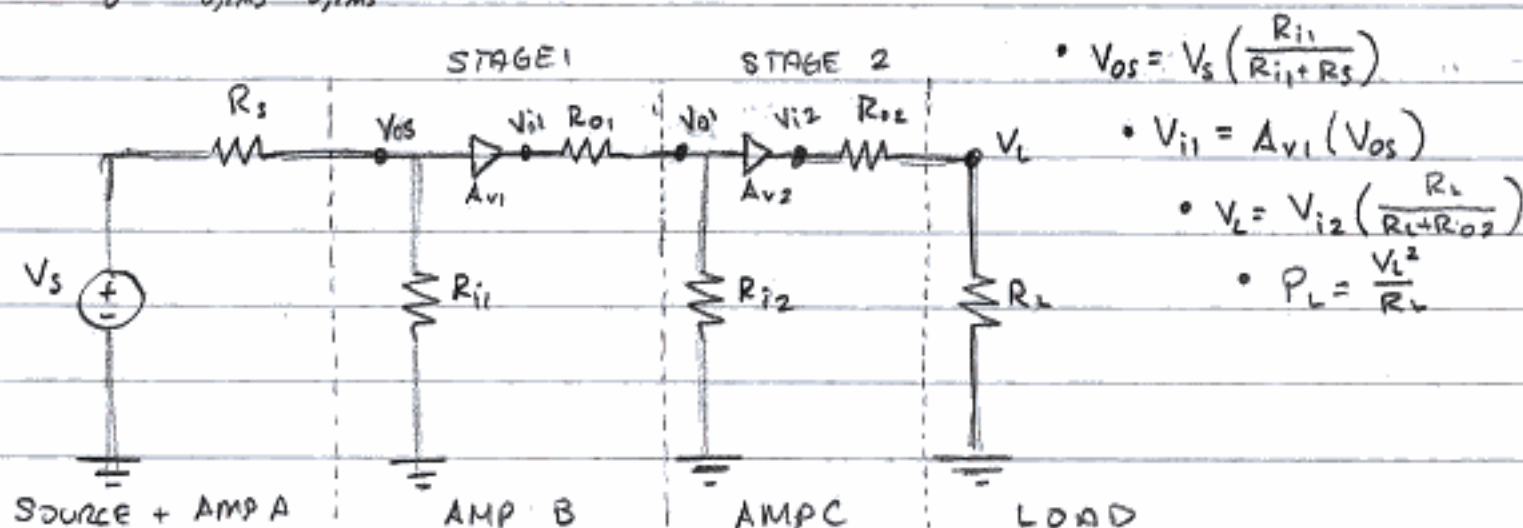
## AMPLIFIERS:

- $P = I_{i,rms} \cdot V_{i,rms}$
- $A_v = \frac{V_o}{V_i}$      $A_p = \frac{P_o}{P_i}$      $A_i = \frac{I_o}{I_i}$     \* OHM'S LAW MAY BE USED TO
- $V_{rms} = \frac{1}{\sqrt{2}} V$     SUB     $V = IR$
- $I_{rms} = \frac{1}{\sqrt{2}} I$
- $10 \log(A_p) = A_p [\text{dB}]$
- $20 \log(A_v) = A_v [\text{dB}]$
- $20 \log(A_i) = A_i [\text{dB}]$
- $10 \log(A_v [\frac{V}{V}] \cdot A_i [\frac{A}{A}]) = A_p [\text{dB}]$
- $P_i = I_{i,rms} \cdot V_{i,rms}$
- $P_o = I_{o,rms} \cdot V_{o,rms}$



\* GIVEN A SIGNAL RANGE,  $V_+ = V_{SUP} - V_{RANGE}$  ,  $V_- = V_{SUP} + V_{RANGE}$