

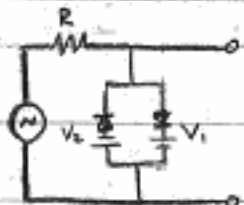

# DIODES AND DIODE CIRCUITS

## DIODE TREES

$V_{max}$   
 $D/R$   
 $D/R$   
 $V_{min}$



- DIODE POINTS AWAY FROM NODE:  $V_o = V_{min}$
- DIODE POINTS TOWARD NODE:  $V_o = V_{max}$
- $I_D = \left( \frac{V_{SOURCE} - V_o}{R} \right)$  (MULTIPLE DIODES AIMED FROM NODE)
- $I_D = \frac{V_i - V_o}{R_i}$  (IF CONDUCTING SINGLE DIODE)
- $I_D = \left( \frac{V_o - V_{SINK}}{R} \right)$  (MULTIPLE DIODES AIMED TO NODE)
- MULTIPLE DIODES: MIN/MAX FROM A DIODED LEG

## BILATERAL LIMITER



$R_f$  = DIODE PROTECTED CUT-IN VOLT.  
 $R_D$  = DIODE FORWARD RESISTANCE

## DIODE CLIPPING


$V_o = \frac{R_D V_i}{R + R_D} + \frac{R V_f}{R + R_D}$
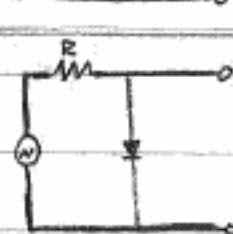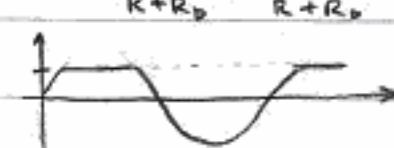
## VOLTAGE CLAMP

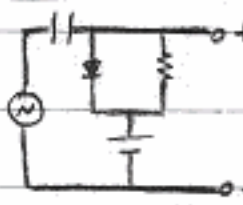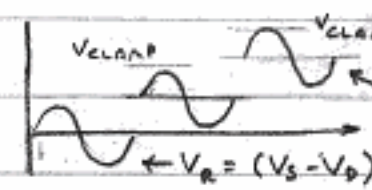



$V_{CLAMP}$   
 $V_R \gg (V_i - V_o)$

## IDEAL VS. ACTUAL

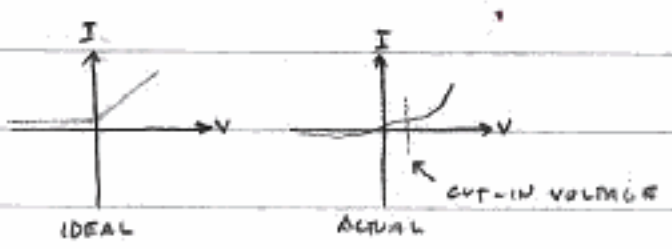

## PEAK DETECTOR

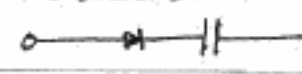
 $I_c(t) = \frac{\partial V}{\partial t}$

## FACTS

- SCHOTTKY DIODE: LOWER VOLTAGE DROP
- CURRENT → LIGHT
- LED: HIGHER  $V_f$
- PHOTODIODE: LIGHT → CURRENT
- PHOTODIODE: ELECTRON RELEASED
- BRIDGE RECTIFIER IS PREFERRED B/C SMALLER CAPACITOR (CHEAPER)
- ZENER DIODES WILL PULL WHATEVER I NECESSARY TO MAINTAIN V

## CHECKS

REVERSE BIAS	$-V_Z \leq V_A \leq 0.7V$
FORWARD BIAS	$V_{AK} \geq 0.7V$
ZENER	$V_{AK} \leq -V_Z$


WHEN CHOOSING DIODES, TWO MAIN CONSIDERATIONS:

1. CURRENT HANDLING CAPABILITIES
2. PEAK INVERSE VOLTAGE


VOLTAGE DIVIDER:  $V_n = \frac{V_s R_n}{\sum R}$


CURRENT DIVIDER:  $I_n = \frac{I_s R_n}{\sum R}$


## PN JUNCTION

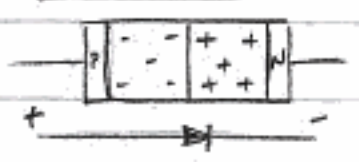

## MISC CIRCUITS

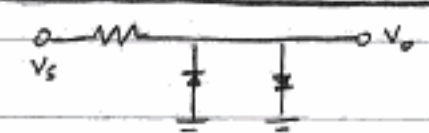

 $V_o = \infty$

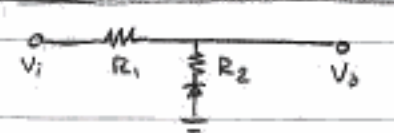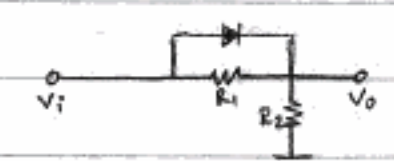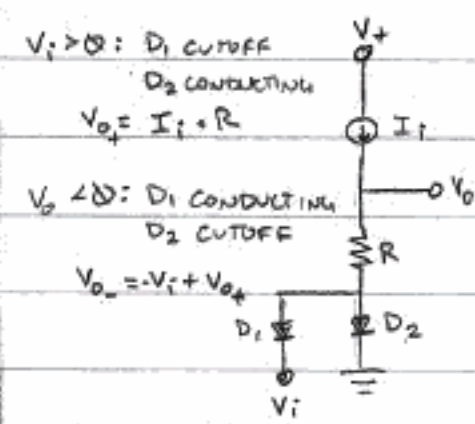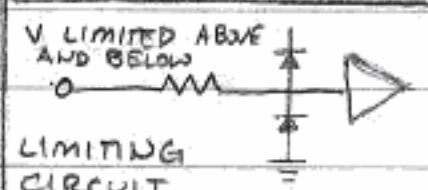

 $V_i < \infty: V_o = \left( \frac{R_2}{R_1 + R_2} \right) V_i$   
 $V_i > \infty: V_o = V_i$




$V_i > \infty: V_o = V_i$   
 $V_i < \infty: V_o = \left( \frac{R_2}{R_1 + R_2} \right) V_i$

$V_i > \infty: D_1$  CUTOFF  
 $D_2$  CONDUCTING  
 $V_o = I_i \cdot R$   
 $V_o < \infty: D_1$  CONDUCTING  
 $D_2$  CUTOFF  
 $V_o = V_i + V_o$



$V$  LIMITED ABOVE AND BELOW  


## ZENER LIMITING CIRCUIT


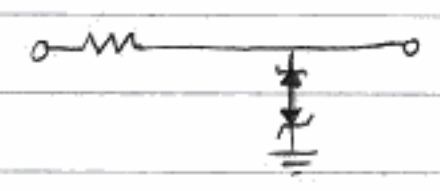


$$V = \sqrt{2} \cdot V_{rms}$$

## PEAK RECTIFIER CIRCUITS

TEST 2 NOTE SHEET



NASH

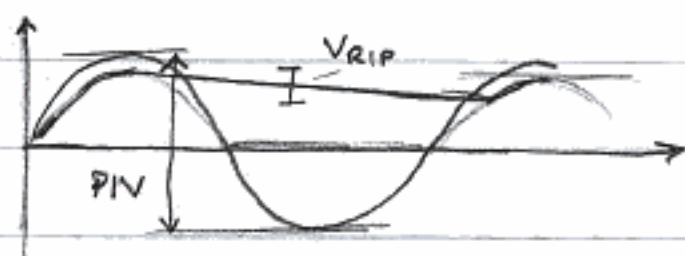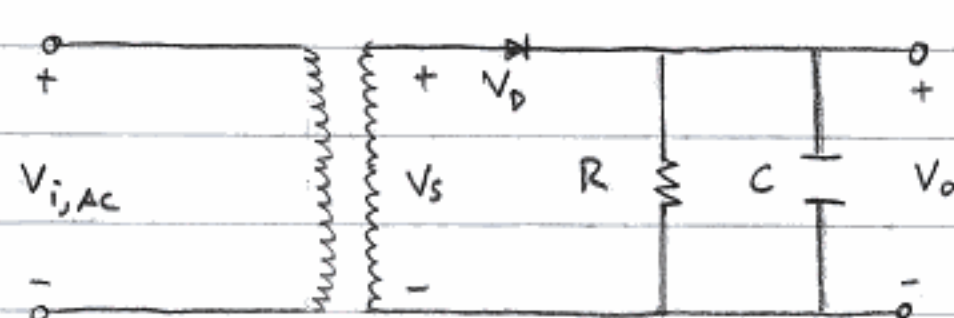

### HALF-WAVE PEAK RECTIFIER

- $V_{RIP} = \frac{V_{max}}{fRC}$
- $V_{max} = \frac{1}{2} V_{RIP} + V_o$
- $V_{PK} = V_o + \frac{1}{2} V_{RIP} + |V_D|$
- $V_{S,rms} = \frac{V_{PK}}{\sqrt{2}}$
- $V_{PK-PK} = |V_{+,PK}| + |V_{-,PK}| + |V_D| + \frac{1}{2} V_{RIP}$
- $PIV = (100\% + x\%)(V_{PK-PK})$
- $I_{D,AVG} = \left(\frac{V_o}{R}\right) \left(1 + \pi \sqrt{\frac{2V_{max}}{V_{RIP}}}\right)$
- $I_L = \frac{V_o}{R}$
- $I_{D,max} = \left(\frac{V_o}{R}\right) \left(1 + 2\pi \sqrt{\frac{2V_{max}}{V_{RIP}}}\right)$

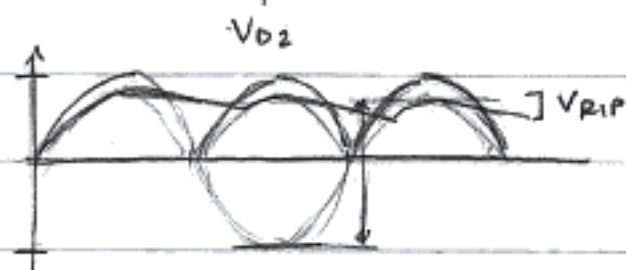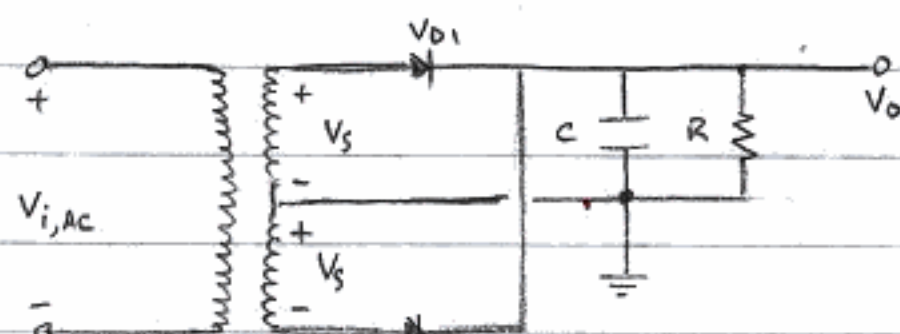\* PIV = PEAK INVERSE VOLTAGE ACROSS DIODE (MAX REVERSE)





### FULL-WAVE PEAK RECTIFIER

- $V_{RIP} = \frac{V_{max}}{2fRC}$
- $V_{max} = \frac{1}{2} V_{RIP} + V_o$
- $V_s = V_{max} + V_D$
- $V_{PK-PK} = 2V_s - V_D$
- $PIV = (100\% + x\%)(V_{PK-PK})$
- $I_{D,AVG} = \left(\frac{V_o}{R}\right) \left(1 + \pi \sqrt{\frac{V_{max}}{2V_{RIP}}}\right)$
- $V_{S,rms} = \frac{2V_s}{\sqrt{2}}$
- $I_{D,max} = \left(\frac{V_o}{R}\right) \left(1 + 2\pi \sqrt{\frac{V_{max}}{2V_{RIP}}}\right)$

EX VALUES:
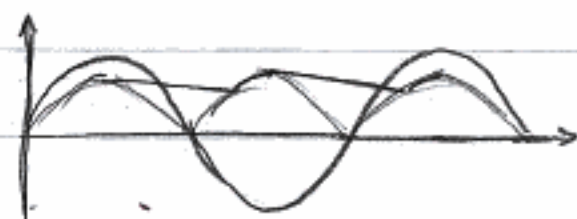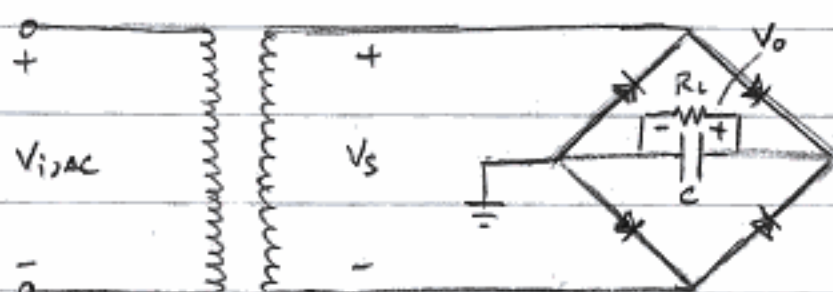
$$\begin{aligned} V_o &= 15V \\ V_{max} &= 16V \\ V_s &= 16.7V \\ V_{PK-PK} &= 32.7V \end{aligned}$$



### FULL-WAVE BRIDGE PEAK RECTIFIER

- $V_s = V_o + \frac{1}{2} V_{RIP} + 2V_D$
- $V_{S,rms} = \frac{V_s}{\sqrt{2}}$
- $V_{RIP} = \frac{V_{max}}{2fCR}$
- $V_{max} = \frac{1}{2} V_{RIP} + V_o$
- $V_{-PK} = -V_{max} - V_D = V_{max, REVERSE}$
- $PIV = (100\% + x\%) |V_{-PK}|$
- $I_{D,AVG} = \left(\frac{V_o}{R_L}\right) \left(1 + \pi \sqrt{\frac{V_{max}}{2V_{RIP}}}\right)$
- $I_{D,max} = \left(\frac{V_o}{R_L}\right) \left(1 + 2\pi \sqrt{\frac{V_{max}}{2V_{RIP}}}\right)$

\*  $I_{D,AVG}$  = AVG I THROUGH DIODE DURING CONDUCTION